

Electricity

Science • Chapter 11 • Chapter Summary & Study Guide for Daksh

Electricity is one of the most important forms of energy in modern life — driving everything from a tube light to a metro train. This chapter develops the basic physics: **electric current**, **potential difference**, **resistance** (Ohm's law), how resistors combine in series and in parallel, and the **heating effect** of current that powers our bulbs and heaters.

Current and potential difference

- **Electric current (I)** — flow of charge per unit time. Unit: **ampere (A)**. $1\text{ A} = 1\text{ coulomb/second}$. Conventional current flows from + to – outside a cell (electrons move opposite).
- **Potential difference (V)** between two points = work done per unit charge moved between them. Unit: **volt (V)**. $1\text{ V} = 1\text{ J/C}$. A cell or battery is a source of potential difference.
- Measured by: **ammeter** (in series, low resistance) for current; **voltmeter** (in parallel, high resistance) for potential difference.

Ohm's law

At constant temperature, the current through a metallic conductor is directly proportional to the potential difference applied across its ends:

$$V = I R$$

where R is the resistance, measured in OHMS (Ω).

$$1\ \Omega = 1\text{ V/A}.$$

Resistance opposes current. It depends on:

- length L (longer wire $\rightarrow$ more resistance)
- area A (thicker wire $\rightarrow$ less resistance)
- material (resistivity ρ)
- temperature (in metals, R increases with T)

$$R = \rho L / A$$

Combination of resistors

- **Series:** resistors joined end-to-end. Same current through all. $R_s = R_1 + R_2 + R_3 + \dots$ (always more than the largest individual).
- **Parallel:** resistors joined between two common points. Same potential difference across all. $1/R_p = 1/R_1 + 1/R_2 + \dots$ (always less than the smallest individual).

In **household wiring**, lights, fans, appliances are connected in **parallel**. Why? Each gets the full supply voltage (220 V); each can be switched on/off independently; if one fails, others keep working.

Heating effect of current

When current flows through a resistor, electrical energy is converted into heat. The amount in time t is:

$$H = I^2 R t = V I t = (V^2 / R) t$$

$$P = V I = I^2 R = V^2 / R \quad (\text{power, in watts})$$

$$1\text{ unit of electrical energy} = 1\text{ kWh} = 3.6 \times 10^6\text{ J}$$

Practical applications: incandescent bulb (tungsten filament — high resistivity and very high melting point $\sim 3380^\circ\text{C}$ — glows brightly when heated white-hot), electric heater, geyser, iron, toaster. **Fuses** use this effect deliberately: a thin alloy (Sn–Pb) wire of low melting point melts when current exceeds the rated value, breaking the circuit and saving appliances/wiring.

Practical pointers and safety

- Power rating of an appliance (e.g. 100 W, 220 V) tells you that at 220 V it draws ~0.45 A.
- Three-pin plugs include an **earth wire** — connects metal body to ground; if a fault occurs and the body becomes live, current escapes safely to earth and protects the user.
- Energy bill is in kilowatt-hours (units), not watts. 1 kWh = 1000 W operated for 1 hour.

★ MUST-REMEMBER POINTS

- $I = Q/t$ (current is charge per second).
- Ohm's law: $V = IR$. R in ohms (Ω). $R = \rho L/A$.
- Series: $R_s = R_1 + R_2 + \dots$; Parallel: $1/R_p = 1/R_1 + 1/R_2 + \dots$
- Household wiring is parallel; each appliance gets full voltage; independent control.
- Heat: $H = I^2 R t$; Power: $P = VI = I^2 R = V^2/R$.
- 1 unit of electricity = 1 kWh = 3.6×10^6 J.
- Fuse melts to break the circuit at excess current — uses heating effect deliberately.

— End of Summary —